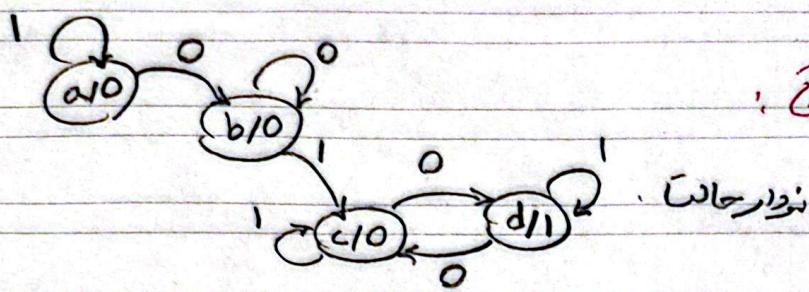


۴۰۳۱۰۸۷۹۳ سمارٹ دیسپلی


آرچیتکچر اول



قرینه هشتم مدارهای منطقی:

نور جادا

(1)

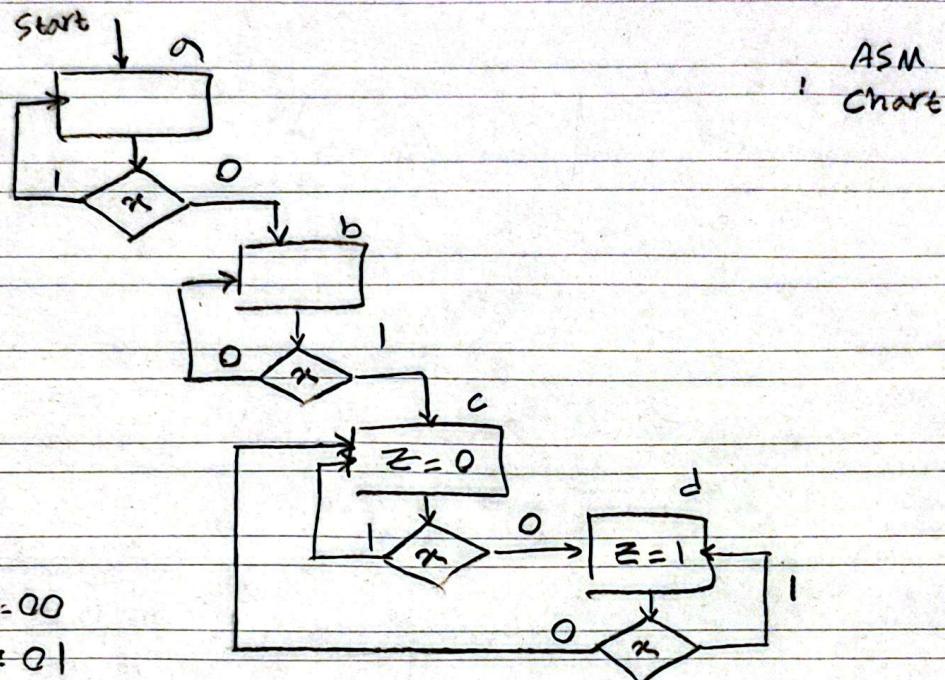

state assignment	$a = 00$
	$b = 01$
	$c = 10$
	$d = 11$

$Q_1 Q_0$

	00	01	1110
0	0	0	1 0
1	1 0	0	1 0

$$Z = Q_1 Q_0$$

P.S. $Q_1\ Q_0$	in n	N.S. $Q_1^+\ Q_0^+$	
		Q_1^+	Q_0^+
0 0	0	0	1 0
0 0	1	0	0 0
0 1	0	0	1 0
0 1	1	1	0 0
1 0	0	1	1 1 0
1 0	1	1	0 0
1 1	0	1	0 1
1 1	1	1	1 1 1


نتیجہ

$Q_1 Q_0$	00	01	11	10
0	0	0	1	1
1	0	1	1	1

$Q_1 Q_0$	00	01	11	10
0	0	1	0	1
1	0	0	1	0

$$Q_1^+ = Q_1 + Q_0 x$$

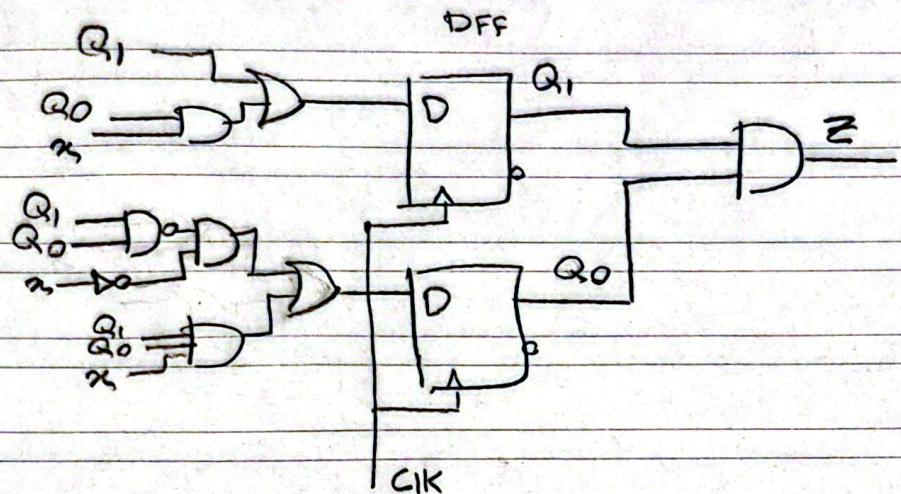
$$Q_0^+ = Q_1' x' + Q_0' x' + Q_1 Q_0 x$$




One Hot: بجزء واحد ملحوظ رأى حالتين حاليتين

D, C, B, A

$$A^+ = A x' + D x$$

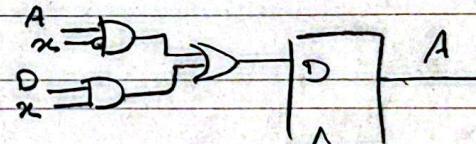


$$B^+ = A x + D x'$$

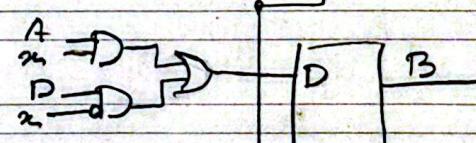


$$C^+ = B + C x'$$




$$D^+ = C x$$

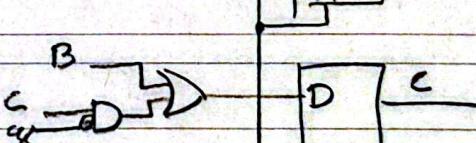


$$Z_1 = B + C x' + D x'$$

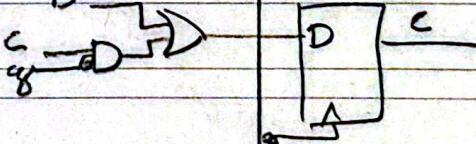

$$Z_2 = C + D x$$

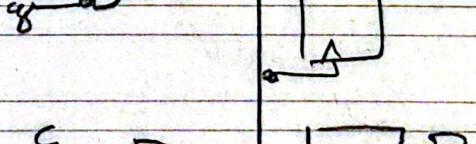

$$Z_1 = B + C x' + D x'$$

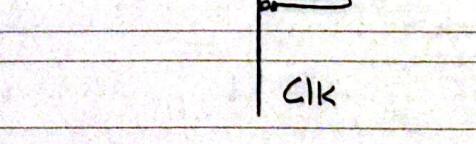

$$Z_2 = C + D x$$


MUX


میکروکنترولر
در مطریجی Q_1, Q_0 میکنترولر

$Q_1 \ Q_0$	Q_1^+	Q_0^+	شرط معکوس	MUX1	MUX0
0 0	0	0	x'	0	x
0 0	0	1	x		
0 1	1	0	1	1	0
1 0	1	0	x'		
1 0	1	1	x	1	x
1 1	0	0	x'	0	x'
1 1	0	1	x		

$$z_1 = Q_1' Q_0 + Q_1 Q_0' x' + Q_1 Q_0 x' = Q_1' Q_0 + Q_0 x' + Q_1 Q_0' x'$$
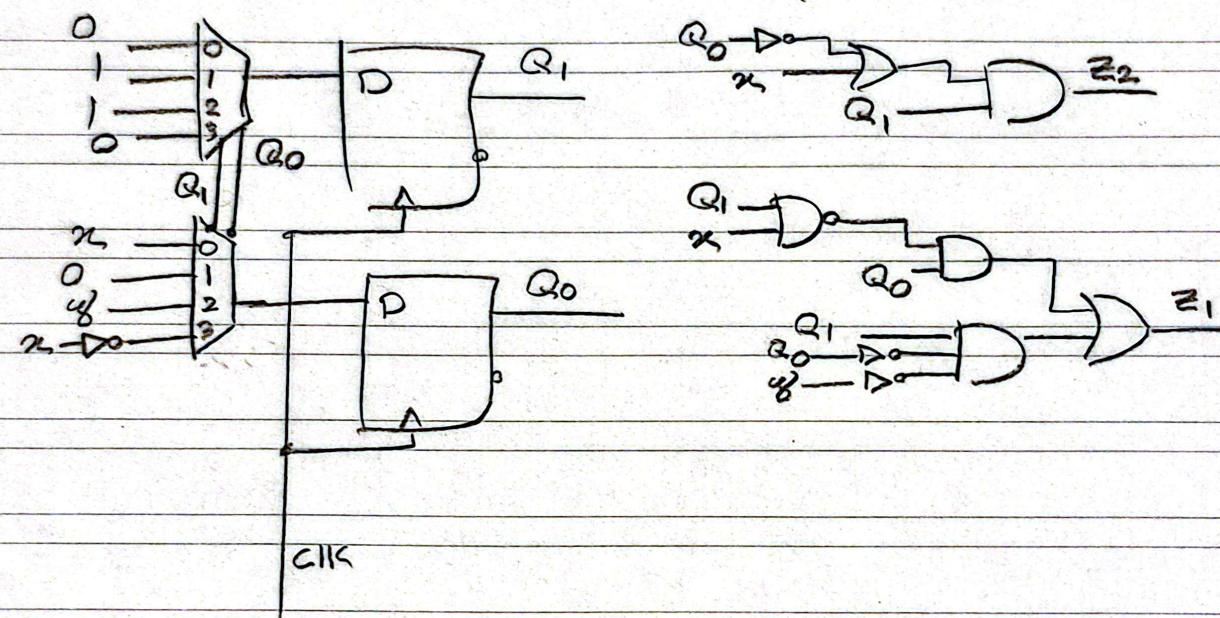
$$z_2 = Q_1 Q_0' + Q_1 Q_0 x = Q_1 (Q_0' + Q_0 x) = Q_1 Q_0' + Q_1 x$$



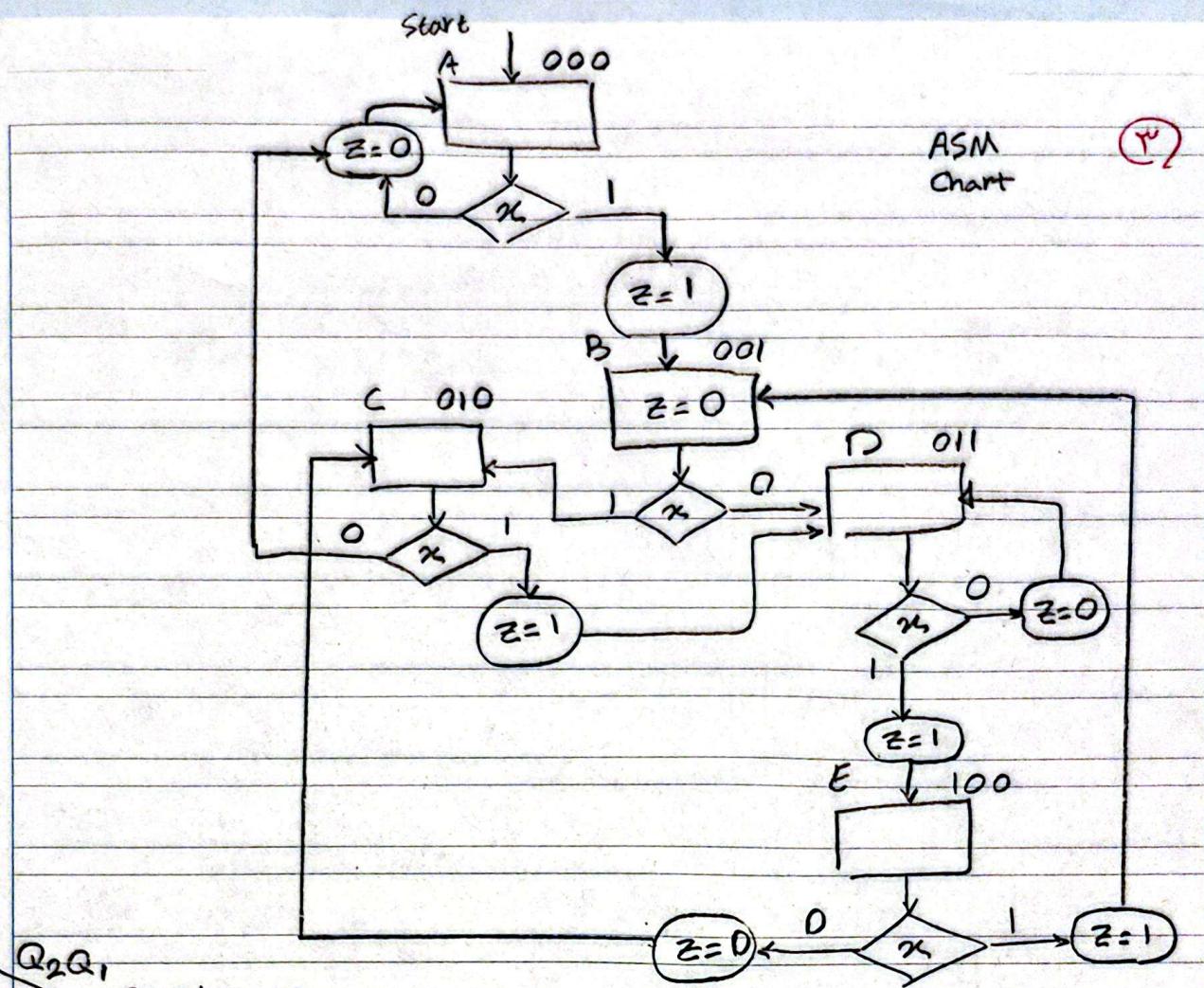

$Q_2 Q_1$	00	01	11	10
$Q_0 x$	00	00 X 0		
α	11 1 X 1			
11	01 X X			
10	00 X X			

$$Z = Q_0' \alpha_3 + Q_1 \alpha_2 = (Q_0' + Q_1) \alpha = B \alpha$$

$f = Q_2' Q_1' Q_0 + Q_2 Q_1' Q_0' + Q_2 Q_1 Q_0'$

Q_2	Q_1	Q_0	x	Q_2^+	Q_1^+	Q_0^+	Z
0	0	0	0	0	0	0	0
0	0	0	1	0	0	1	1
0	0	1	0	0	1	1	0
0	0	1	1	0	1	0	0
0	1	0	0	0	0	0	0
0	1	0	1	0	1	1	1
0	1	1	0	0	1	1	0
0	1	1	1	1	0	0	1
1	0	0	0	0	1	0	0
1	0	0	1	0	0	1	1

$Q_2 Q_1$

$Q_0 x$	00	01	11	10
00	0	0	x	0
01	0	0	x	0
11	0	1	x	x
10	0	0	x	x

 $Q_2 Q_1$

$Q_0 x$	00	01	11	10
00	0	0	x	1
01	0	1	x	0
11	1	0	x	x
10	1	1	x	x


$$Q_2^+ = Q_1 Q_0 x$$

$Q_2 Q_1$	00	01	11	10
$Q_0 x$	00	0	x	0
00	0	0	x	0
01	1	1	x	1
11	0	0	x	x
10	1	1	x	x

$$Q_1^+ = Q_0 x' + Q_1' Q_0 + Q_1 Q_0' x + Q_2 x'$$

$$Q_0^+ = Q_0' x + Q_0 x' = Q_0 \oplus x$$


$$D_2 = Q_2^+ = Q_1 Q_0 x = D x$$

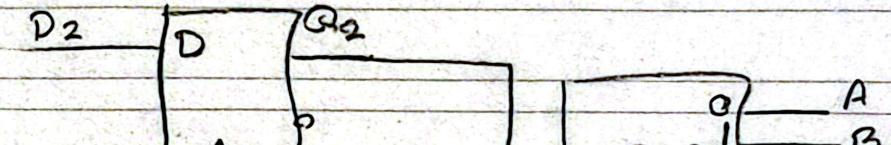

$$\begin{aligned} D_1 &= Q_1^+ = (B + D)x' + B \\ &+ Cx + Ex' = \\ &B + Cx + Dx' + Ex' \end{aligned}$$

$$D_0 = Q_0^+ = Q_0 \oplus x =$$

$$(B + D) \oplus x$$

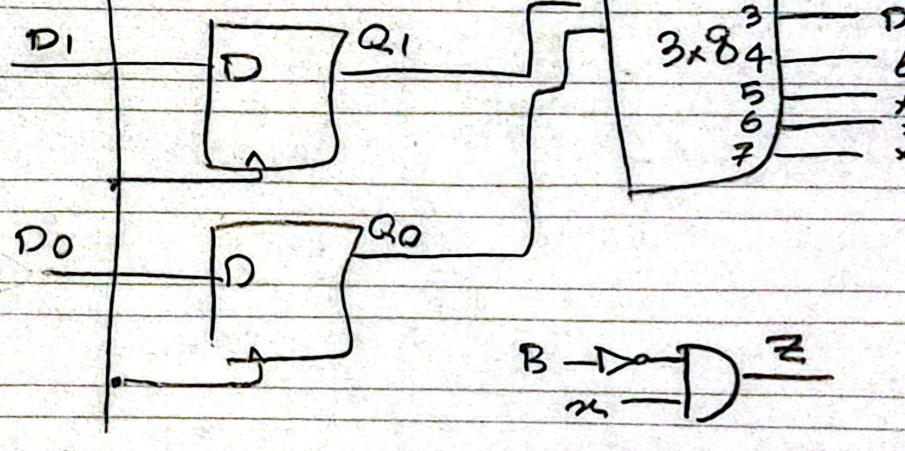

P.S.


N.S.

out


حول حالت


حالات
الحالات

	$\alpha=0$	$\alpha=1$	
000	000	001	0
001	010	011	0
010	100	101	0
011	110	111	0
00	000	001	0
101	010	011	1
110	100	101	1
111	110	111	0

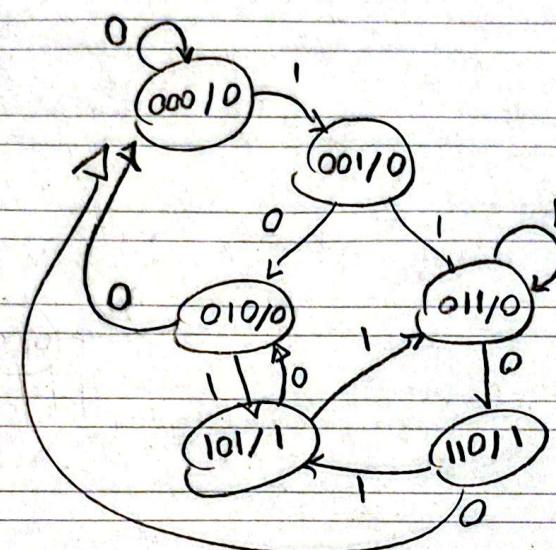

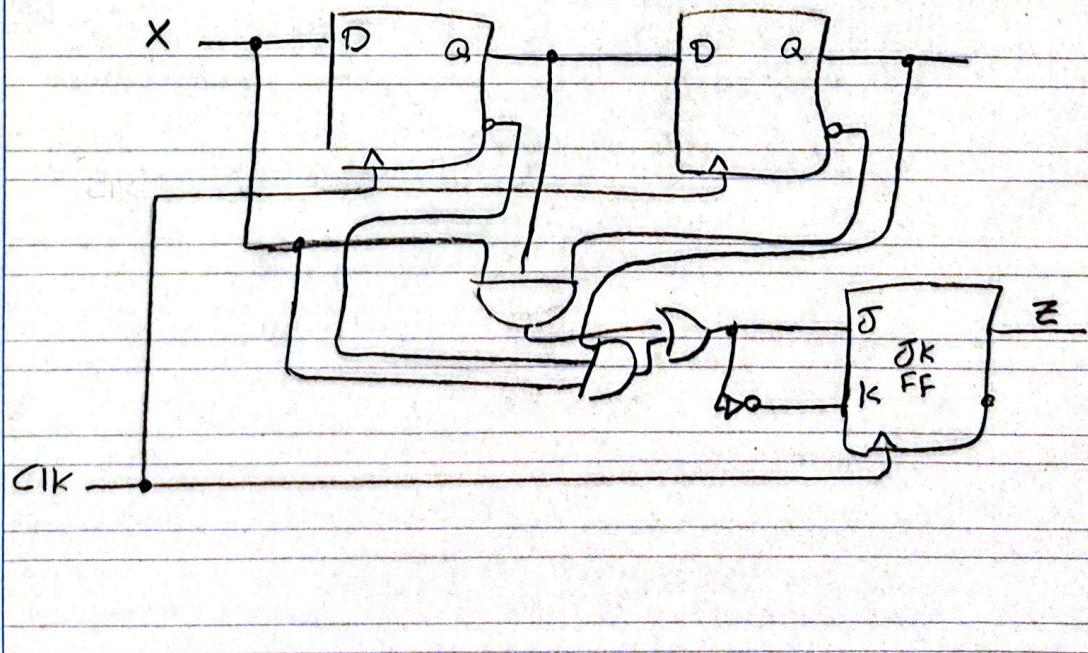
روش حافظه محدود ، سیکل بینبرای DFF و JKFF



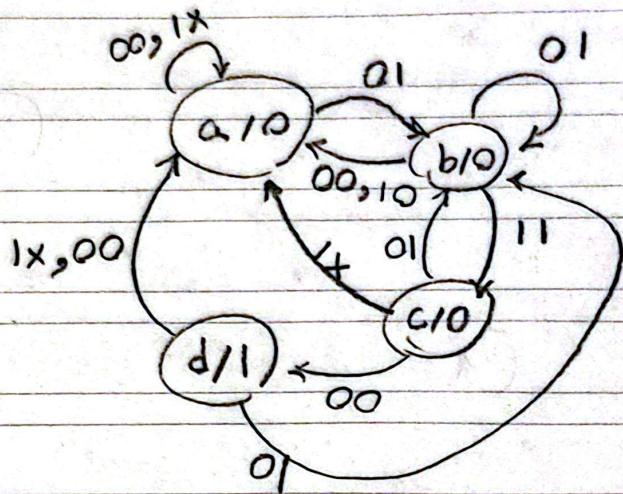

(b)

موجز

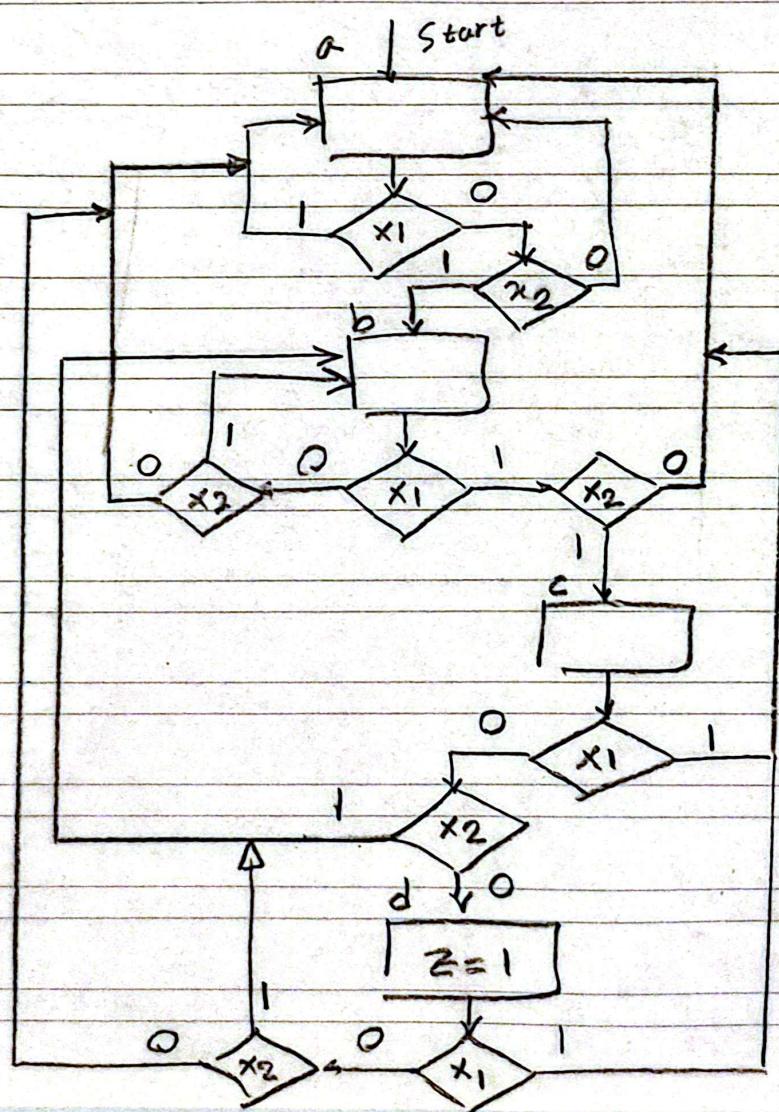

موجز

a: 00 b: 01 c: 10 d: 11 $\bar{Q}_1 \bar{Q}_0$ \bar{w}_{12}

$Q_1 Q_0 x_1 x_2$	$Q_2^+ Q_1^+$	$Q_1 Q_0$
0 0 0 0	0 0	00 01 11 10
0 0 0 1	0 1	00 00 0 1
0 0 1 X	0 0	01 00 0 0
0 1 0 0	0 0	11 01 0 0
0 1 0 1	0 1	10 00 0 0
0 1 1 0	0 0	
0 1 1 1	1 0	
1 0 0 0	1 1	
1 0 0 1	0 1	$Q_2^+ = Q_1 Q_0' x_1' x_2 + Q_1' Q_0 x_1 x_2$
1 0 1 X	0 0	00 00 0 1
1 1 0 0	0 0	01 11 1 1
1 1 0 1	0 1	11 00 0 0
1 1 1 X	0 0	10 00 0 0

$$Z = Q_1 Q_0$$

$$Q_0^+ = x_1' x_2 + Q_1 Q_0' x_1'$$

